

DAMSIC Questions

An Open-Source Summary

Thomas Debelle

Sjouke Spijkerman

Robin Geens

Sander Crols

June 24, 2025

Contents

Recap of questions per chapter	1
S&H	1
DAC	1
ADC	1
$\Sigma - \Delta$	1
Voltage ref	2
Oscillator	2
Tuned Amplifiers	2
DCDC	2
Wireline	2
Optical	2
H05E3A - Exam Questions	3

Recap of questions per chapter

S&H

Q	page	Q	page
1	19	2	31
3	44		

DAC

Q	page	Q	page
4	16-17	5	28
6	36		

ADC

Q	page	Q	page
7	9-11	8	38
9	40-41	10	56
11	63	12	71
13	89		

$\Sigma - \Delta$

Q	page	Q	page
14	35,42,45	15	53
16	11,37,46	17	46-48
18	64-65	19	11,37
20	XX		

Voltage ref

Q	page	Q	page
21	18	22	29

Oscillator

Q	page	Q	page
23	XX	24	44
25	XX	26	XX
27	28	28	45

Tuned Amplifiers

Q	page	Q	page
29	XX	30	27
31	38	32	XX

DCDC

Q	page	Q	page
33	1:23	34	1:29
35	1:48	36	2:14
37	2:34		

Wireline

Q	page	Q	page
38	XX	39	16
40	XX	41	XX
42	27		

Optical

Q	page	Q	page
43	30-39	44	XX
45	XX		

This section is based on the previous work of *Robin Geens* and *Sander Crols*. Sjouke and I added new questions and answered them partially. I used notebook LM on top of already answered questions to add more informations and verified its output.

H05E3A - Exam Questions

Here is a comprehensive response to your query, drawing on the provided sources:

1. Describe the pedestal step and a possible solution for the problem.
 - **Pedestal Step and Solution:** The **pedestal step** is a non-ideality observed in Sample and Hold (S&H) circuits, appearing as an **abrupt change in the output voltage** (V_{out}) during the transition from the sampling phase to the hold phase. This effect is visually represented as a sudden upward or downward jump in the V_{out} waveform at the moment the input signal is sampled. It is primarily caused by **charge injection from the channel** and by **parasitic capacitance between the gate and output** from the switch as it turns off, specifically due to the switch's drain-capacitance and unintended coupling.
 - A possible solution for pedestal step compensation involves using **half-sized dummy switches**. These dummy switches are designed to absorb the charge from the main switch, thereby reducing the unwanted pedestal step. For this method to work effectively, the charge must split approximately 50% between the main and dummy switches. However, the success of this compensation technique is critically dependent on the **careful timing of clock edges**. If there are unequal impedances on the left and right sides of the main switch, or if clock edges are too fast, it can lead to an unequal charge split, which will diminish the effectiveness of the compensation. Therefore, ensuring that the **impedances are as equal as possible** is crucial for optimal compensation.
2. Discuss the need for bootstrapped switches in switched-capacitor circuits.
 - The main issue is the fact that $R_{on} \propto 1/V_{gs}$. So by changing the input voltage we change the RC time constant and so it creates **DISTORTION** which is highly unwanted in TH circuits. Solution \rightarrow Keep it constant using **bootstrapping** aka keep a constant V_{gs} .
 - So we need to keep V_{gs} high to avoid any saturation. The higher the V_{gs} the smaller the R_{on} resistance. We first need to do a hold phase on the cap to charge it up to V_{dd} then in the track phase that input voltage is added on top of the cap.
 - Challenges: make sure the body diodes do not open which will result in current to substrate, charge lost and latch-up !
 - **Need for Bootstrapped Switches in Switched-Capacitor Circuits:** Bootstrapped switches are important components in switched-capacitor (SC) circuits, particularly when **high accuracy** is required. In the context of Delta-Sigma converters, for example, they are specifically utilized **at high accuracies** to mitigate the effects of **clock feedthrough**.
3. Discuss offset and noise in the flip-around T/H circuit.
 - With a regular T&H circuit, the signal transfer function should be 1. This means that the sampling capacitor should be equal to the feedback capacitor. This results in a feedback factor of 1/2, so a closed loop gain of two.
 - An alternative is the flip-around T&H, which uses no feedback capacitor. During both phases, the opamp is in unity gain feedback. The offset and low frequency noise are cancelled out, because they affect both the V_{C_hold} and the output voltage. The high frequency noise is amplified by a factor of two.
 - The offset voltage cancels out because the opamp creates its own virtual ground in both phases. Noise transfer function from opamp input node to output. The sampled thermal noise on C_{hold} is still present.
 -
4. Discuss the effect of the impedance variation in a resistor ladder in resistive DACs
 - **Effect of Impedance Variation in Resistor Ladder DACs:** In resistive Digital-to-Analog Converters (DACs) employing a resistor ladder, the output impedance exhibits a significant variation with the input code. This variation is characterized as a **parabolic function**. The equivalent resistance ($R_{eq}(m)$) can be calculated using the formula $R_{eq}(m) = \frac{m(2^N - m)}{2^{N+1}} R_{tot}$, where m is the digital input code and 2^N is the total number of resistors. The maximum equivalent resistance, equal to $0.25 \cdot R_{tot}$, occurs at the midpoint of the digital range.
 - This **parabolic variation of impedance** has several detrimental effects on the DAC's performance:
 - It leads to **signal-dependent current delivery**, meaning the current supplied to the load changes non-linearly with the input signal. In other terms **DISTORTION**

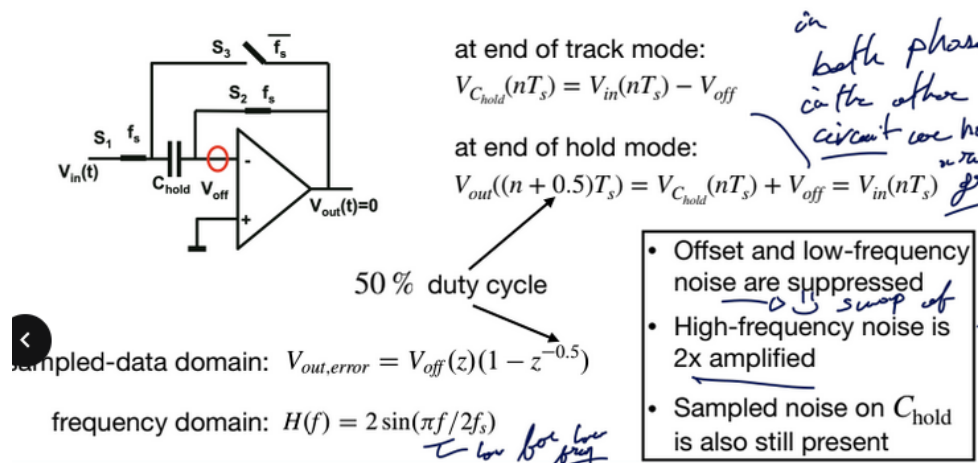


Figure 1: Equations for Flip around

- For a fixed capacitive load, the **time constant becomes signal-dependent**, which affects the settling behavior of the DAC output.
- Collectively, these signal-dependent characteristics introduce **distortion at high frequencies**, degrading the overall linearity and dynamic performance of the DAC.

5. Discuss the common-centroid layout in the framework of current-steering DACs.

- Current steering DAC can be unary or binary. Unary are preferred for MSB to avoid big current switch off and on and binary for LSB.
- Current steering DACs (unary) are very sensitive to mismatches. Instead of using matrix decoding, where all sources are placed sequentially (according to bit order) in a grid, issue:
 - Doping, oxide thickness not constant
 - PSS drop
 - Clock timing
 - Temperature
- they can be placed according to a common-centroid layout. This layout is symmetrical in both dimensions. **Any linear gradient in the production process is cancelled** out by the fact that two opposing sources are used (vertical, horizontal and slant). The addressing of the sources is less straightforward than with matrix decoding.
- To go even further, every current cell can be subdivided and distributed across the array with some Q^2 schemes which improve reliability against second order effect.

6. Describe the problem of stray capacitances in the design of capacitive DACs.

- Problem of Stray Capacitances in Capacitive DACs:** Stray capacitors are capacitance from the switches right next to the (binary scaled) capacitors. The stray capacitor at the left poses no problem (not added to output). The charge of the right one is added to the feedback capacitor, which means that the total charge transferred is no longer correct. The problem can be solved by using four switches per capacitor instead of two.
- In the charge phase, the first stray cap is charged but not the right one. The trick in the transfer phase is that the charged left cap will have both inputs connected to the same V_{ref} so it will discharge onto this. Thanks to the virtual ground of the opamp, the right cap will not be charged making the error 0.
- Right stray is never charged (thanks to virtual ground of the AMP) and left one will charge and discharge on itself

7. What limits the regeneration in a latch-based comparator, and how can it be improved?

- Comparators are difficult blocks as we need **High BW, high AMP, High Accuracy, Wide range, Low power** so latch helps with it thanks to a feedback loop but we need a David Goliath latch to still be able to change the value on it. Latch is better than cascade of amp as cascading amp is **SLOWWWWW** + Memory effect.
- 2 phase latch with first pre-amp and then latch behavior.
- Limits to Regeneration in Latch-Based Comparators and Improvements:** In a latch-based

comparator, the regeneration process, where a small input difference is amplified to a full digital output, is characterized by an exponential growth of the differential voltage $V(t)$ across the latch outputs, given by $V(t) = \alpha V_{LSB} e^{+t/\tau}$. The regeneration speed is fundamentally determined by the **time constant** $\tau = C/g_{m,l}$, where C is the parasitic capacitance at the output nodes and $g_{m,l}$ is the transconductance of the latch's gain stage. Pre amp $\rightarrow A_{pre} = \frac{g_{min}}{C} T_{pre}$

- The regeneration in a latch-based comparator is limited by three regimes based on the input differential voltage (ΔV_{in}):
 - **High ΔV_{in} :** The regeneration time is limited by the inherent **propagation delay** of the latch circuit. \rightarrow Tech constant max speed
 - **Medium ΔV_{in} :** The comparator operates within the **exponential regime**, where the signal grows exponentially. \rightarrow Take a bit of time to get the result $\tau \approx 10ps$.
 - **Small ΔV_{in} :** In this critical regime, **noise dominates the input**, leading to potential errors in the decision-making process. This is closely related to the phenomenon of **metastability**, where the comparator fails to produce a stable output within the required time, resulting in an ambiguous output. Metastability can lead to conversion errors in Analog-to-Digital Converters (ADCs).
- To improve regeneration performance and mitigate metastability errors:
 - One can **reduce the effective number of bits (N)** in the converter, or conversely, **increase the sampling period (T_s)**, which effectively reduces the operating speed. \rightarrow longer Pre-amp stage to avoid the small ΔV_{in} .
 - Another approach is to **reduce the time constant τ** . This can be achieved by decreasing the parasitic capacitance C or increasing the transconductance $g_{m,l}$ of the latch (so higher power consumption, wider NMOS, weak inversion).
 - While metastability is a critical issue for general comparators, in Delta-Sigma ($\Delta\Sigma$) converters, it is considered “**not an issue**” for the comparator itself because any comparator error will be shaped and subsequently filtered. However, it is essential to ensure that the digital bit fed to the decimation filter is the same as the one fed to the DAC, which typically requires placing a **synchronization latch**.

8. How can averaging improve the performance of a flash ADC?

- A flash Analog-to-Digital Converter (ADC) utilizes $2^N - 1$ comparators to convert an analog input into an N-bit digital word. A major non-ideality in flash ADCs is **comparator offset**, which results in non-ideal thresholds and contributes to differential non-linearity (DNL) errors.
- While direct “averaging” of multiple comparator outputs for improved resolution or linearity is not explicitly described, the following related techniques are mentioned that contribute to better performance:
 - **Auto-zeroing schemes:** These techniques are employed to **cancel comparator offset** and suppress both offset and low-frequency noise within individual comparators. This can be seen as a form of “temporal averaging” or correction within each comparator.
 - **Comparator with Offset Cancellation:** An approach for open-loop comparator offset cancellation involves selecting a subset (e.g., “four-out-of-eight minimally sized input pairs”) from multiple input pairs. While not explicitly stated as averaging their outputs, this selection process aims to achieve a more ideal performance by potentially averaging out random offsets across a pool of devices.
 - **Majority voting:** In the context of Successive Approximation Register (SAR) ADCs, it's mentioned that **majority voting** can be used to mitigate **comparator noise**. While stated for SAR ADCs, the principle of using multiple decisions to reduce noise and errors could conceptually be applied to other ADC architectures like flash ADCs if multiple comparator outputs are available and processed.
- Offset of the comparators in a flash ADC can cause linearity problems and lead to DNL/INL. The effect of offset can be reduced by coupling the comparators so that multiple input pairs are used for every decision. This is done with resistive coupling, so that neighboring decisions influence each other. This helps because the signals at the outputs of the comparators add up linearly, but the offsets will add up with root mean square. The overall signal-to-offset ratio will thus increase. The comparator will ‘appear much larger’.
- More area needed, more power consumption.

9. Discuss the folding technique, its advantages, and challenges.

- In a folding circuit, multiple input pairs are cross coupled to ‘fold’ the linear input voltage of a regular comparator. This reduces the range, so less comparators are needed to convert the output of the folding circuit to bits. The conversion is divided into a coarse part (the folding itself, pre-processing) and a fine part (flash conversion of the folding output). This reduces the amount of input pairs: $2^3 + 2^5$ instead of 2^8 . One input pair of the folding circuit will be active (other ones saturated) and which pair will determine the MSB’s.
- The desired transfer curve of the folding circuit contains non-linearities in the peaks (**distortion at crossover points**). It is not possible to realize this in practice, so when the input voltage is in this range, it will be distorted. A solution to this is by using double the amount of input pairs in two folding circuits. Then we either **interpolate** those two folding circuits or take the one that is working in its **linear** region.
- There is some delay, and we need some good amplifier to realize the fine conversion.

 


Figure 2: Folding circuits

•

10. **Advantages and Disadvantages of a 1.5-bit Pipeline Converter Compared to a 1-bit Pipeline Converter:**

Pipeline converters break down the analog-to-digital conversion into multiple stages, each processing a certain number of bits. The comparison between 1-bit and 1.5-bit stages primarily revolves around trade-offs in speed, complexity, and accuracy.

1-bit Pipeline Converter:

- Straight forward, check if value is above or below $V_{ref}/2$, multiply by 2, next stage, repeat. If an error before, will ripple through the chain.
- **Advantages:**
 - **Maximum speed:** With its subrange limited to a single bit, it typically uses an amplifier with a 2x gain, which can achieve high conversion speeds.
 - **Intrinsic linearity:** The 1-bit DAC in its feedback loop is inherently linear, contributing to the overall intrinsic N-bit precision of the converter. A 1-bit DAC is always perfectly linear, and time-domain converters leverage this for excellent linearity.
 - **Simplicity:** Requires only a single comparator for its analog-to-digital conversion within each stage.
 - The basic building block is a Multiplying Digital-to-Analog Converter (MDAC).
- **Disadvantages:**
 - **Delay:** The full digital value is available after $N+3$ clock periods, as each stage processes one bit sequentially. This delay, while exchanged for speed, can be problematic in feedback loops.
 - Potentially more stages required for a given resolution compared to multi-bit stages, which could increase overall complexity and power (though per-stage power is low).
 - **Good and accurate settling in all the stages**

1.5-bit Pipeline Converter (a type of Multi-Bit MDAC Pipeline Converter):

- Will have $\pm V_{ref}/4$ if 2 positive decision, subtract V_{ref} , 2 negative add V_{ref} else do nothing.
-
-

1.5-Bit Pipeline Stage

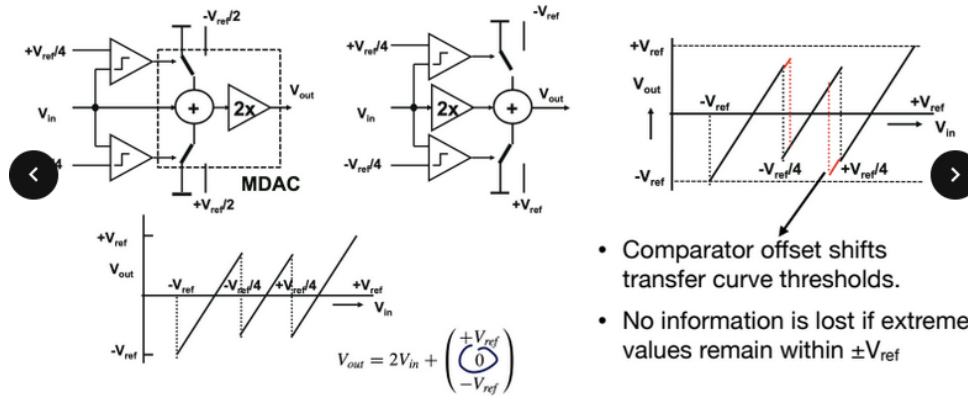


Figure 3: Offset doesn't impact precision since added reliability

 


Figure 4: Redundancy

- **Advantages:**

- **More aggressive stage-scaling:** By processing more than one bit per stage (e.g., 1.5 bits, 2.5-4 bits), these converters allow for a reduction in the total number of stages required for a given resolution. This can lead to more compact designs.
- **Error Correction Margin:** Having more levels per stage (e.g., six segments for 2.5 bits) provides a margin to correct errors that might occur in the comparators.
- **Higher Overall Performance:** Can achieve higher effective number of bits (ENOB) at comparable or higher sample rates compared to purely 1-bit per stage designs, as seen in examples where 2.5-bit stages are used at the front-end followed by 1.5-bit stages.

- **Disadvantages/Challenges:**

- **Slower amplifier settling:** Due to the higher gain required in multi-bit stages (e.g., 4x or 8x gain), the amplifiers need more time to settle accurately.
- **More complex DACs:** The first stage requires a multi-level DAC (e.g., a five-level DAC for a 2.5-bit stage) that must maintain the **full accuracy of the entire converter**. This multi-bit DAC is a critical component and its non-linearity due to mismatch can be a significant problem.
- **Increased Complexity for DAC Linearity:** Mismatch in multi-bit DACs can generate non-linearity errors. Techniques like **Data Weighted Averaging (DWA)** are used to make these errors noise-like so they can be filtered by oversampling, resulting in much lower harmonic distortion. This adds complexity to the digital processing.
- Offset is not removed and we hope that the redundancy will help. Or high-freq noise amplified

11. Opamp Sharing Technique in Pipeline Converters

The opamp sharing technique in pipeline converters allows a single operational amplifier (opamp) to be used in two subsequent stages of the converter. This approach is implemented by adapting the Multiply-Digital-to-Analog Converter (MDAC) structure to share the opamp between channels.

The main advantage of this technique is a **significant reduction in power consumption, often by a factor of 2x**. However, this comes with certain trade-offs:

- **Offset voltage is not compensated.** No auto-zeroing technique
- It can introduce a **memory effect between subsequent samples**.
- It is only feasible if the opamp is not required to create a virtual ground during its operation.

12. Differences Between Top-Plate and Bottom-Plate Sampling

In the context of charge-redistribution converters, sampling involves connecting the input signal to a capacitor bank. The sources describe two primary methods:

Top-Plate Sampling:

- **No attenuation of the sampled voltage** occurs.
- However, it causes an **attenuation of the reference voltage**.
- The Most Significant Bit (MSB) can be determined directly after sampling.

Problematic for high accuracy as not same attenuation between ref and input but faster.

Bottom-Plate Sampling:

- This method results in **the same attenuation for both the input and reference voltages**.
- A key advantage is that the **input voltage range can be made equal to the reference voltage range**.
- A common-mode voltage (VCM) is employed to maintain the comparator input at the desired level.

Trickier setup with the common mode, will be slower but really good for high accuracy ADC. We have a precharge phase.

13. Comparison of Dual-Slope Converter with a Straightforward Slope Converter

Both dual-slope converters and straightforward slope (or linear approximation/counting) converters belong to the category of linear search converters. They differ significantly in their operation and characteristics:

Straightforward Slope (Linear Approximation/Counting) Converter:

- **Operation Principle:** The converter uses a counter to linearly increase the output of a Digital-to-Analog Converter (DAC). A comparator continuously compares this increasing DAC output (V_{DAC})

with the sampled input signal (V_{signal}). Once V_{DAC} exceeds V_{signal} , the comparator toggles, and the current counter value is stored as the digital output; the counter is then reset.


- **Conversion Time:** The output is ready after 2^N **clock cycles**, where N is the number of bits. This is considerably slower compared to flash (1 clock cycle) or pipeline (N clock cycles) converters.
- **Input Handling:** An input Sample & Hold (S/H) circuit is required to keep the input signal constant during the conversion period.
- **Offset:** The comparator offset can be added to the digital output code. Usually we first convert known ref signal then measure actual signal and subtract both of them.
- **Applications:** Often used in applications like image sensor readouts, where one ADC per column shares a DAC and counter. Small transistors in comparators in such applications can lead to offset and $1/f$ noise, necessitating correlated double sampling to measure a known reference and the signal, then digitally subtract the values. Can be used as a tracking converter with minimum changes.

Dual-Slope Converter:

- **Operation Principle:** This converter operates in two distinct phases:
 1. **Integration Phase:** The input signal is integrated for a fixed sample period.
 2. **Discharge Phase:** The integrated capacitor is then discharged by a fixed reference current. The time taken for discharge is proportional to the integrated input signal, and this time is measured to determine the digital output.
- **Conversion Time:** The conversion time is typically $(2 \cdot 2^N)/f_s$, making it suitable for slowly varying input signals.
- **Offset Cancellation:** A significant advantage is that **offsets are cancelled** due to the two-phase operation, as the same integrator and comparator are used for both the input signal and the reference current. This is an example of a “zero-crossing method” where linearity is primarily required around the zero level.
- **Linearity:** Linearity is only required around the zero level for the comparison, as the unknown signal is determined by comparing it to an equivalent signal from the DAC.

 14. Why are 1st order or higher-order single-loop sigma-delta topologies not advised?

Higher order loops are not inherently stable. Every low pass filter adds a ninety-degree phase shift which means that anything above second order can become unstable. Need a precise b_1 to counter balance and stabilize the loop.



- We can increase the noise shaping by increasing the order
- Second order \rightarrow unstable
 - Need b_1 to stabilize

Figure 5: Second order issue

Stability can be shown with the limit cycle and we see that it shouldn't spiral out. If it spirals out, it will get limited by PSS and so create **distortion**.

In the derivation of the sigma delta converter, we assumed a white noise distribution. This assumption is not correct for first order $\Sigma - \Delta$ converters. There is a lot of clicking and **pattern noise** because of deterministic quantization noise. This creates a **dead zone** in the DC function that spans 2 - 3 bits. Noise shaping doesn't work anymore

In higher order topologies, the intermediate signals must become smaller to limit signal swing after the next integrator. This means that the SNR ratio is inherently reduced. (not a problem in feedforward topologies) Furthermore, higher order topologies are unstable for certain combinations of filter coefficients.

This makes the implementation very difficult. Truly dependent of the implementation and precision of the weights.

If there is an interest in increasing the order of a $\Sigma - \Delta$ converter, MASH converters are advised that cascade multiple lower order modulators and will decorrelate noise from its signal without becoming more unstable (n 1st order loops, instead of 1 nth order loop)

15. Explain the principle of data-weighted averaging.

Data-Weighted Averaging (DWA) is a noise shaping technique used in oversampling applications. Its main idea is to **modulate the error**. In a multi-bit Digital-to-Analog Converter (DAC) within the feedback path of a Delta-Sigma converter, mismatch between DAC elements can generate non-linearity errors.

While simple offset errors can be easily “chopped” (a modulation technique) and filtered by the zeros in the decimation filter, the errors caused by mismatch in multi-bit DACs are signal-dependent, leading to distortion. DWA addresses this problem by making these signal-dependent errors **noise-like**, allowing the oversampling process to filter them off.

DWA will cycle through the cells and so will smooth out the error, it will transform the distortion into an equivalent white noise pattern. It is the same idea as for SD

16. Discuss the advantages and disadvantages of single-bit and multi-bit sigma-delta converters.

Using a higher order (stability problems with classical topology so use cascade) or using multi-bit DACs in the feedback path.

Single-bit Sigma-Delta Converters:

- **Advantage:** A 1-bit DAC (Digital-to-Analog Converter) is **inherently linear**. This eliminates non-linearity errors that can arise from element mismatch in multi-bit DACs in the feedback path.

Multi-bit Sigma-Delta Converters:

- **Advantages:** indicating high performance in these areas, especially compared to “Single Loop” and “Cascade”. Multi-bit converters, particularly Delta-Sigma converters with low Over-Sampling Ratio (OSR), are considered suitable for “High-Resolution High-Speed AD converters”.
- **Disadvantage:** The main problem with multi-bit Delta-Sigma converters is the **linearity of the multi-bit DAC in the feedback path**. Mismatch between the individual DAC elements will generate non-linearity errors. Techniques like Data-Weighted Averaging (DWA) are employed to mitigate this issue by making the signal-dependent error noise-like so it can be filtered out by oversampling. Typically we need a DAC in the return which was not needed in 1-bit ADC !
- **Solutions:** can use chopping, dynamic element matching. Offset is okay if we can one time add it then remove it so on average it is null and can be seen as a noise that the OSR nature of SD will take care of.

17. Explain limit cycles in delta-sigma converters. Why do we need them but why do we want them to be random?

- **The problem:** If there is **no noise** and the input signal to a Delta-Sigma converter is a “static” or near-DC signal, the “white noise approximation” for quantization does not hold up, and oversampling alone does not help in noise reduction. In such cases, the quantization error might become correlated with the input, leading to **predictable, undesired tones or patterns in the output spectrum** instead of spread-out noise. This is what is typically referred to as **limit cycles or idle tones**. Also they should be stable and non-repetitive to avoid distortion.
- **The solution/why we want them random:** If they are not random, they will lead to a 2-3 bits LSB blindness. To overcome this limitation, the system needs to “store the error and add it to the previous sample”. More broadly, the idea is to ensure that the quantization error is random and wideband, so it can be shaped and filtered.

18. Describe CIC decimation filters and their latency when used in an incremental converter.

A CIC (Cascaded Integrator-Comb) filter is a simple (only additions/subtractions!) and efficient decimation filter used in SD converters. It consists of integrator stages followed by comb (differentiator) stages and acts like a low-pass sinc filter to remove out-of-band quantization noise while reducing the sample rate.

$$T_{\text{avg}} = \left(\frac{1}{M} \frac{1 - z^{-M}}{1 - z^{-1}} \right)^n = \frac{1}{M} \left(\frac{1}{1 - z^{-1}} \right)^n \left(\frac{1 - z^{-M}}{1} \right)^n$$

 


Figure 6: CIC filter

In incremental sigma-delta converters, which operate over short measurement windows, CIC filters are still used for decimation, but their latency matters. The output becomes valid only after the full integration and comb operation is complete, resulting in a latency of roughly

$$(n + 2) \cdot OSR \cdot 2 \cdot T_s = \text{latency} \quad [\text{time}]$$

Where n is the number of stages. The factor 2 comes from one cycle for integration, and one cycle for differentiation. Per sample an integration and decimation is needed. It is based on the sinc function which in frequency domain is an ideal brick wall filter. The idea is to combine integrator and differentiator.

19. What is the advantage of oversampling sigma-delta techniques for the design of the anti-alias filters? What is the difference between discrete and continuous time DS converters?

- **Advantage of oversampling for anti-alias filters:** In Delta-Sigma converters, **oversampling** is a fundamental principle that allows the quantization noise to be spread over a wider frequency band. This noise is then shaped, meaning it's pushed out of the desired signal band. The "loop filter" within the Delta-Sigma modulator helps in this noise shaping. As a result, the demanding requirements on the **anti-alias filter** are relaxed. For example, a **continuous-time Delta-Sigma converter itself can function as an anti-alias filter**, which also helps in saving power. This is because the oversampling and noise shaping inherently provide significant attenuation for out-of-band signals, reducing the need for a steep, high-order external analog anti-alias filter.

When no oversampling is used, the input signal should not have frequencies larger than $f_s/2$. Otherwise, the higher frequency components will be folded on top of the lower ones when the signal is sampled, which results in aliasing. This LPF should ideally be a perfect brick-wall filter with a cutoff frequency of $f_s/2$. This is not possible to realize in practice.

With an oversampling converter, the sampling happens at a higher frequency than the Nyquist frequency. Frequency components (a bit) higher than Nyquist frequency will not result in aliasing. This relaxes the requirements of the analog low-pass filter while spreading out the noise quantity. The converted digital signal will be down sampled to return to the Nyquist frequency, and this might result in aliasing if the signal is not properly filtered first. But this filtering operation can be done in the digital domain, which is easier.

In continuous-time converters, the loop filter runs continuously using resistors, capacitors, and amplifiers. This gives a natural anti-aliasing effect without extra filtering stages and saves power, but comes with drawbacks: it's more sensitive to clock jitter, component variation (like resistor mismatch), and offers less flexibility for tuning or reconfiguration.

– **Difference between discrete and continuous time DS converters:**

- * The sources implicitly differentiate between discrete and continuous-time Delta-Sigma (DS) converters.
- * A **continuous-time Delta-Sigma converter** has the advantage that its loop filter **can also function as an anti-alias filter**, potentially saving power. However, it is susceptible to clock jitter, which can add noise, and the use of resistors for feedback (to combat jitter) can lead to wide variations over different process corners and a less **flexible architecture**.
- * **CHECK LECTURE CAUSE I AM PRETTY SURE HE SAID SOMETHING**

20. What happens if, instead of a lowpass filter, a bandpass filter is used as noise shaping filter in a sigma-delta ADC?

If a **bandpass filter** is used as the noise shaping filter (also referred to as the "loop filter") in a Delta-Sigma ADC, the system becomes a **bandpass delta-sigma converter**. This means that instead of pushing the quantization noise to high frequencies (as a low-pass noise shaping filter does), the noise is shaped and moved away from a specific central frequency band, concentrating the signal within that band. An advantage of this approach is that **demodulation can be done directly on the bitstream in the**

digital domain using simple operations like multiplication by +1 or -1. This implies that a bandpass Delta-Sigma ADC is suitable for signals that are already modulated around a carrier frequency, removing the need for a separate mixer.

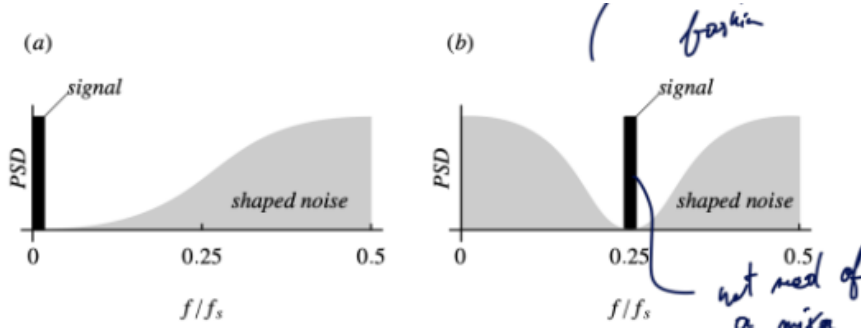


Figure 7: Band pass

21. Schematic of a Low Voltage Bandgap with Folded Resistors

 


Figure 8: Folded resistors low voltage bandgap

The sources present a schematic for a low voltage bandgap reference which incorporates “folded resistors” and sums proportional to absolute temperature (PTAT) and complementary to absolute temperature (CTAT) components in the current domain. This design addresses the challenge of implementing a 1.2V silicon bandgap in a 1.2V technology, such as 65nm.

The circuit shown (identified as a “Static Start-up circuit” but also appearing as the core bandgap circuit) consists of:

- **Bipolar Junction Transistors (BJTs) Q1 and Q2:** These generate the temperature-dependent voltages. Q1 has a scaling factor of $\langle 1 \rangle$ and Q2 has a factor of $\langle 1 : N \rangle$, indicating that Q2 is N times larger than Q1, or that N unit transistors are used for Q2. The difference in their base-emitter voltages, ΔV_{BE} , is proportional to absolute temperature (PTAT).
- **Resistors R1 and R2:** R1 is used to generate the PTAT current. R2 generates a current that is complementary to absolute temperature (CTAT), as it is connected in series with Q1, whose V_{BE} exhibits a negative temperature coefficient.
- **Operational Amplifier (OpAmp):** The OpAmp forces the voltage at its two input terminals to be equal. In this circuit, one input is connected to the collector of MP1 and the other to a node between R1 and the emitter of Q2.
- **PMOS Transistors MP1 and MP2:** These act as current mirrors. MP1 mirrors a current derived from Q1 and R2, while MP2 receives current from the node where R1, Q2, and the OpAmp’s negative input connect.

Current Generation and Summation: The circuit operates by generating two primary currents:

- **I_{CTAT} (Complementary To Absolute Temperature):** This current is defined as $I_{CTAT} = \frac{V_{BE1}}{R_2}$. Since V_{BE} decreases with increasing temperature, I_{CTAT} will also decrease with increasing temperature.
- **I_{PTAT} (Proportional To Absolute Temperature):** This current is defined as $I_{PTAT} = \frac{\Delta V_{BE}}{R_1}$. The difference in base-emitter voltages (ΔV_{BE}) between Q1 and Q2, due to their emitter area ratio, is proportional to absolute temperature. Thus, I_{PTAT} increases with increasing temperature.

The design “is adding ptat and ctat in the current domain”. The total output current, I_{OUT} , is the sum of these two currents: $I_{OUT} = \frac{V_{BE1}}{R_2} + \frac{\Delta V_{BE}}{R_1}$. By appropriately sizing R_1 , R_2 , and the BJT area ratio (N), these two temperature-dependent currents can be made to cancel each other’s temperature dependency, resulting in a temperature-independent output current.

The “folding of resistors” is mentioned as a technique similar to that used in folded cascode operational transconductance amplifiers (OTAs). This technique can allow the circuit to operate with a lower supply voltage (e.g., $V_{DD} < 1V$ for CMOS bandgaps), as it reduces the required voltage headroom by allowing different parts of the circuit to operate at different voltage levels without stacking them directly.

Finally, a temperature-independent reference voltage, V_{ref} , is generated by passing the stable I_{OUT} through an additional resistor R_3 : $V_{ref} = R_3 I_{OUT}$. If R_2 and R_3 are designed as multiples of R_1 (i.e., $R_2 = n_2 R_1$ and $R_3 = n_3 R_1$), the reference voltage can be expressed as

$$V_{ref} = V_{BE1} \frac{n_3}{n_2} + \Delta V_{BE} n_3$$

22. Why are Voltage References More Accurate than Current References?

- **Voltage References (Vref):** Bandgap voltage references are described as being based on a “physical constant,” which contributes to their high accuracy. The silicon bandgap voltage is approximately 1.2V. This inherent physical property provides a robust and predictable reference. While factors like matching, ratio accuracy, and curvature correction (to linearize temperature dependence) are important design considerations, the core reference relies on a fundamental material constant. We can match the CTAT with the PTAT making it reliable. Moreover, the resistance do not really matter, we keep them unit and enhance the matching like this.
- **Current References (Iref):** In contrast, current references are stated to be “Based on Vref and R”. The crucial distinction is that they have “No physical parameter” directly underlying their value, leading to “limited accuracy”. While current references also involve considerations such as matching, ratio accuracy, and curvature correction, their ultimate stability and accuracy are inherently tied to the stability and accuracy of the voltage reference they are derived from, as well as the precision of the resistor used. Resistive elements can have variations in their sheet resistance (e.g., Poly, p+, p-well resistors have absolute tolerances of 30%, 22%, and 66% respectively) and temperature coefficients (e.g., 0.2, 0.4, and 2 for the temperature exponent α in $R = R_{300}(T/300)^\alpha$). These variations can directly impact the accuracy of a current reference that relies on them. Accuracy of current source can be as low as $\pm 35\%$.

In summary, bandgap voltage references leverage a fundamental and stable physical property of silicon, making them inherently more accurate. Current references, however, are typically *derived* from a voltage reference and a resistor, introducing additional dependencies and potential inaccuracies from the resistor’s characteristics.

23. Why do we need an amplitude control loop in the design of a Xtal oscillator?

An amplitude control loop is crucial in the design of a Crystal (Xtal) oscillator due to significant variations that can occur during the production process. When designing a Xtal oscillator under nominal conditions, there can be **huge variations in production**, specifically:

- +/- 20% in capacitance.
- +/- 20% in transconductance (gm).

These production variations can lead to several problematic conditions for the oscillator:

- The oscillator may **fail to start up**.
- The **drive power might exceed the rated limits of the crystal**, potentially causing lifetime issues for the crystal.

To mitigate these issues, especially when considering performance variations “over corners” (referring to different operating conditions and manufacturing variations), an amplitude control loop must be implemented. This ensures that the **amplitude is regulated**, preventing excessive power consumption and crystal damage while guaranteeing reliable startup. Without it, if the transconductance (gm) is too high ($gm > gm_{opt}$), more power is consumed to compensate for Rs, and if gm exceeds a certain critical value ($gm > gm_A$), the amplitude will grow until the average gm drops back to gmA, which can lead to **distortion due to non-linear behavior**.

24. Describe the design of a Pierce oscillator.

The sources outline key considerations for designing a **Crystal (Xtal) oscillator**, which commonly refers to a Pierce oscillator configuration, as indicated by the typical circuit diagram. The design process involves balancing several factors to ensure stable oscillation and desired performance.

Key design parameters and considerations:

- **Crystal parameters:** Start with the specific parameters of the crystal, including its series resonance frequency (f_s), parallel resonance frequency (f_p), series resistance (R_s), and parallel capacitance (C_p).
- **Capacitor selection:**
 - **C3:** This capacitor should be chosen to be greater than the crystal's parallel capacitance (C_p), approximately 1 pF higher, to accommodate parasitic capacitances.
 - **C1 and C2:** These capacitors should be significantly larger than C3 ($C_1, C_2 \gg C_3$) to achieve a **low pulling factor**. The pulling factor determines how much the oscillation frequency can be shifted by varying the load capacitance. However, there's a trade-off: larger C1 and C2 also lead to higher drive power, so their values must be limited. It's also important to account for parasitic capacitances from external pins, which can be at least 10 pF.
- **Resonance type:** The goal is to achieve **series resonance**.
- **Transconductance (gm):**
 - Calculate the **minimum required gm (gmA)**, also referred to as **gm_crit**, to ensure oscillation. If gm is less than gmA, no oscillation will occur.
 - For reliable startup margin, it is recommended to use a gm value that is **10 times gmA**.
- **Bias and Amplitude:**
 - **Vgs-VT:** This voltage is determined based on the acceptable distortion, phase noise (lower swing typically increases phase noise due to the post-amplifier), and the desired drive level.
 - **Ibias:** Calculate the bias current based on the chosen Vgs-VT.
 - **Amplitude Control Loop:** As discussed previously, an amplitude control loop is essential to manage maximum power levels across different manufacturing corners, preventing crystal damage and ensuring consistent operation.

25. How to create a ring oscillator with a quadrature output?

A standard ring oscillator typically consists of an odd number of inverters connected in a loop, which produces a single oscillating output. To create a ring oscillator with a **quadrature output (90-degree phase difference)**, the sources indicate using **differential amplifiers** instead of simple inverters.

Here's how it works:

- Instead of standard inverters, use **differential inverting amplifiers** as the stages of the ring oscillator.
- By **cross-coupling** the outputs from one stage to the inputs of a subsequent stage in a specific way, it becomes possible to use an **even number of amplifier stages**. This setup inherently allows for the generation of signals that are 90 degrees out of phase, thus providing quadrature outputs.
- Differential inverting amplifiers also offer advantages such as **high Power Supply Rejection Ratio (PSRR)** and **high Common Mode Rejection Ratio (CMRR)**. Using amplifiers with **low gain** can help to smoothen the edges of the output signal, leading to lower distortion.

26. Why doesn't the noise of the VCO contribute to the output phase noise at low offset? Can you make a connection with other parts of the course?

In a Phase-Locked Loop (PLL) system, the Voltage Controlled Oscillator (VCO) noise does not significantly contribute to the output phase noise at low offset frequencies *within the loop bandwidth* because of the **filtering action of the PLL's loop filter**.

A PLL typically consists of a Phase Detector, a Charge Pump, a Loop Filter, and a VCO. The loop filter, often incorporating a charge pump and a capacitor, provides an integrating function ($1/s$). When combined with the integrating characteristic of the VCO itself (which translates a control voltage into a frequency, and thus integrates frequency deviations to produce phase, leading to another $1/s$ in the phase domain), the overall open-loop transfer function can have an s -squared term ($1/s^2$), which is important for stability.

The **loop bandwidth** (e.g., 35 kHz for an integrated loop filter) defines the range of frequencies over which the PLL effectively tracks the reference signal. Inside this bandwidth, the loop acts as a **low-pass filter for the reference noise** and a **high-pass filter for the VCO's intrinsic noise**. Therefore, at low offset frequencies (i.e., within the loop bandwidth), the **phase noise of the reference signal** dominates the output phase noise, while the **VCO's own noise is suppressed** by the feedback action. Conversely, outside the loop bandwidth, the VCO's noise contributions become more significant because the loop can no longer track and suppress them effectively.

Connecting this to general course concepts, this phenomenon is a direct application of **feedback control theory** and **noise shaping in closed-loop systems**. The loop filter's design (e.g., using an R-C network, although the source notes "problem of noise!" with simple R-C) dictates the loop's bandwidth and its ability to suppress in-band noise from the VCO while maintaining stability and tracking the reference. The concept of how a feedback loop's bandwidth determines which noise sources dominate at different offset frequencies is fundamental in control systems and signal processing, ensuring that the output frequency precisely follows the reference frequency and that internal noise is attenuated within the desired band.

27. **Explain the operating principle of a fractional-N PLL.**

The provided sources discuss various components of a Phase-Locked Loop (PLL), such as the phase detector, charge pump, loop filter, and Voltage Controlled Oscillator (VCO). It also mentions the need for adaptive frequencies in real systems through tuning, calibration, and clock recovery, where a VCO serves as the basic building block of a PLL.

However, the sources **do not contain any information or explanation regarding the specific operating principle of a fractional-N PLL**. They describe general PLL components and their roles but do not delve into the fractional-N architecture or its mechanism for achieving non-integer frequency division ratios.

28. **Discuss the sizing of the biasing transistors in a relaxation oscillator. Explain why a capacitor at the drain of the bias transistor can degrade the duty cycle.**

Regarding the sizing of biasing transistors in a relaxation oscillator, the sources **do not provide specific details on how to size the biasing transistors in a relaxation oscillator**. While discussions on I_{bias} and $V_{\text{GS}} - V_{\text{T}}$ are present in the context of a Pierce (crystal) oscillator, outlining their impact on transconductance (g_m) and ensuring startup margin, this information is not directly translatable to the specific design considerations for biasing transistors within a relaxation oscillator, nor does it detail sizing methodologies for such. The sources only mention that "Relaxation oscillators have too much phase noise", but do not delve into their architectural design or component sizing.

Concerning why a capacitor at the drain of the bias transistor can degrade the duty cycle: The sources indicate a general relationship in oscillators where a **high oscillation amplitude can lead to distortion**, and this distortion, in turn, can result in a **non-50% duty cycle**. While the sources do not explicitly detail the specific mechanism by which a capacitor at the drain of a bias transistor in a relaxation oscillator causes this degradation, they do establish the link that **excessive amplitude (potentially influenced by circuit components like capacitors or biasing arrangements) directly contributes to waveform distortion, which deviates the duty cycle from its ideal 50% value**. A well-designed oscillator aims for a specific amplitude to balance desired signal integrity with power consumption and phase noise. If the presence or value of a capacitor at the drain of a bias transistor contributes to an uncontrolled or excessively high oscillation amplitude, this can lead to the observed duty cycle degradation due to the resultant non-linear operation of the oscillator circuit. For instance, if the current is too high in a circuit, it can lead to higher distortion in the output waveform.